

Redstone circuits/Pulse

[Edit article feedback](#)[< Redstone circuits](#)

A **pulse circuit** is a [redstone circuit](#) which generates, modifies, detects, or otherwise operates on redstone pulses.

Contents

Pulses

[Pulse logic](#)[Pulse interactions](#)[Pulse analysis](#)

Monostable circuit

Pulse generator

[On-pulse Generator](#)[Circuit Breaker Pulse Generator](#)[Observer Pulse generator](#)[Dust-Cut Pulse Generator](#)[NOR-Gate Pulse Generator](#)[Locked-Repeater Pulse Generator](#)[Comparator-Repeater Pulse Generator](#)[Off-pulse Generator](#)[OR-Gate Off-Pulse Generator](#)

Pulse length limiter

[Off-pulse limiter](#)

Pulse extender

Pulse multiplier

[Split-path pulse multiplier](#)[Enabled-clock pulse multiplier](#)[Triggered-clock pulse multiplier](#)

Pulse divider

Edge detector

[Rising edge detector](#)[Falling edge detector](#)[Dual edge detector](#)[Inverted rising edge detector](#)[Inverted falling edge detector](#)

[Inverted dual edge detector](#)

[Pulse length detector](#)

[Transports and Logic gates implemented in Pulse logic](#)

[References](#)

[Navigation](#)

Pulses

A **pulse** is a temporary change in redstone power that eventually reverts to its original state.

An **on-pulse** is when a redstone signal turns on, then off again. On-pulses are usually just called "pulses" unless there is a need to differentiate them from off-pulses.

An **off-pulse** is when a redstone signal turns off, then on again.

The **pulse length** of a pulse is how long it lasts. Short pulses are described in [redstone ticks](#). For example, a "3-tick pulse" is a pulse that turns off 0.3 seconds (or 6 game ticks) after it turns on. Longer pulses, meanwhile, are measured in any convenient unit of time (for example, a "3-second pulse").

The **rising edge** of a pulse is when the power turns on – the beginning of an on-pulse or the end of an off-pulse.

The **falling edge** of a pulse is when the power turns off – the end of an on-pulse or the beginning of an off-pulse.

Pulse logic

Pulse logic is a different approach to binary logic than standard redstone power binary (power present = 1, power absent = 0). In pulse logic, the pulse is a toggle of logic level of the contraption: (first pulse = 1, second pulse = 0). This approach allows implementing computational logic that operates not only on redstone signal, but also on block updates, and block positions; in particular implementation of mobile logical circuits in [flying machines](#), and significant reduction of server-side lag through avoiding redstone dust, transporting signals through block updates instead - e.g. over [Powered Rail](#). In many cases use of pulse logic also results in more compact circuitry, and allows building 1-tileable modules where classic redstone power would "spill" to the neighbor modules.

Conversion from classic redstone binary to pulse logic is performed through dual edge detectors, (usually just an [Observer](#) observing redstone dust or other power components), and conversion back is performed through [T flip-flop](#) circuits, in particular the block-dropping behavior of sticky pistons. That behavior is also utilized as memory storage in pulse logic, position of the block encoding state of memory cell.

Pulse interactions

Some redstone components react differently to short pulses:


- In *Java Edition*, a piston or sticky piston usually takes 1 tick to extend. If the activation pulse ends before the extension does, the piston or sticky piston "aborts" – it places the first of the pushed blocks at its final position (only if it's a sticky piston) and return to its retracted state instantly. This can cause sticky pistons to "drop" their block – they push a block and then return to their retracted state without pulling it back.
- A redstone comparator does not always activate when given a 1 tick pulse and never activates when given pulses shorter than 1 tick.
- A redstone lamp can be deactivated only by an off-pulse of minimum 2 ticks.
- A redstone repeater does increase the length of pulses which are shorter than its delay to match its delay (for example, a 4-tick repeater changes any pulse shorter than 4 ticks into a 4-tick pulse).
- In *Java Edition*, a redstone torch does not always activate when given a 1 tick pulse and never activates when given pulses shorter than 1 tick.

Pulse analysis

When building circuits, it can sometimes be helpful to observe the pulses being produced to confirm their duration or spacing.

A pulse can be measured with 1-tick precision with an **oscilloscope** (see schematic, right).

An oscilloscope simply consists of a line of 1-tick repeaters (aka a "racetrack"). An oscilloscope should be constructed to be at least as long as the expected pulse, plus a few extra repeaters (the more repeaters, the easier it is to time capturing a pulse). For periodic pulses (as from clock circuits), an oscilloscope should be at least as long as the clock period (both the on and off parts of the pulse).

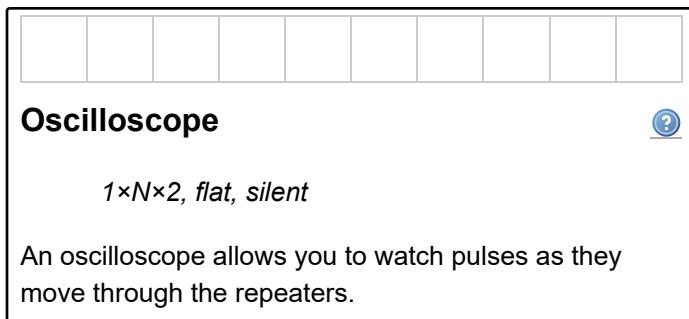

An oscilloscope can be frozen to aid reading by:

- using an oak sign next to the design.
- positioning the oscilloscope on the screen so that it can be viewed when the player pauses the game, or
- taking a screenshot with **F2**, or
- running repeaters into the side of the oscilloscope and powering them simultaneously to lock the repeaters of the oscilloscope.

An oscilloscope is not capable of displaying fractional-tick pulses directly (0.5-tick pulses, 1.5-tick pulses, etc.), but for fractional-tick pulses greater than 1 tick, the pulse length may appear to change as it moves through the oscilloscope. For example, a 3.5-tick pulse may sometimes

power 3 repeaters and sometimes 4 repeaters.

Half-tick pulses do not vary between powering 0 or 1 repeaters (they just look like 1-tick pulses), but half-tick and 1-tick pulses can be differentiated with a [redstone comparator](#) – a 1-tick pulse can activate a comparator, but a half-tick pulse cannot in most cases.

Multiple oscilloscopes can be laid in parallel to compare different pulses. For example, you can determine a circuit's delay by putting the circuit's input signal through one oscilloscope and the circuit's output through another and counting the difference between the input and output signal edges.

Oscilloscopes are useful but sometimes require you to be in an inconvenient position to observe them. If you just need to observe the simultaneity of multiple pulses it can be useful to use pistons or note blocks and observe their movement or note particles from any angle. Redstone lamps are less useful for this purpose because they take 2 ticks to turn off.

Monostable circuit

A circuit is **monostable** if it has only one stable output state ("mono-" means "one", so "monostable" means "one stable state").

A circuit's output can be powered or unpowered. If an output stays in the same state until the circuit is triggered again, that output state is called "stable". An output state that changes without the input being triggered is not stable (that doesn't necessarily mean it's random – it may be an intentional change after a designed delay).

If a circuit has only *one* stable output state then the circuit is called "monostable". For example, if a powered state inevitably reverts to the unpowered state, but the unpowered state doesn't change until the input is triggered.

When someone says "monostable circuit" in *Minecraft*, they usually mean a [pulse generator](#) or a [pulse limiter](#). However, any redstone circuit which produces a finite number of pulses is technically a monostable circuit (all the circuits in this article, in fact, as well as some others), so instead of saying monostable circuit, it can be helpful to be more specific:

- A [pulse generator](#) generates a pulse
- A [pulse limiter](#) reduces the duration of long pulses
- A [pulse extender](#) increases the length of short pulses
- A [pulse multiplier](#) produces multiple output pulses in response to a single input pulse
- A [pulse divider](#) produces an output pulse after a specific number of input pulses
- An [edge detector](#) produces an output pulse when it detects a specific edge of an input pulse
- A [pulse length detector](#) produces an output pulse when it detects an input pulse of a specific length
- A [block update detector](#) produces an output pulse when a specific block is updated (for example, stone is mined, water turns to ice, etc.)
- A [comparator update detector](#) produces an output pulse when a specific comparator is

updated by an inventory update

Clock circuits also produce pulses, but they aren't monostable because they have *no* stable output states (they are "astable") unless forced into one by external interference (for example, when they're turned off). Logic and memory circuits aren't monostable because *both* of their output states are stable (they are "bistable") – they don't change unless triggered by their input.

See also: [Wikipedia:Monostable](#)

Pulse generator

A **pulse generator** creates an output pulse when triggered.

Most pulse generators consist of an input and a [pulse limiter](#). A [pulse extender](#) can be added on to generate a longer pulse.

Schematic Gallery: Pulse Generator


On-pulse Generator

Circuit Breaker Pulse Generator

*1×3×3 (9 block volume), 1-wide
circuit delay: 1 tick
output pulse: 1 tick*

The circuit breaker is one of the most commonly used pulse generator due to its small size and adjustable output.

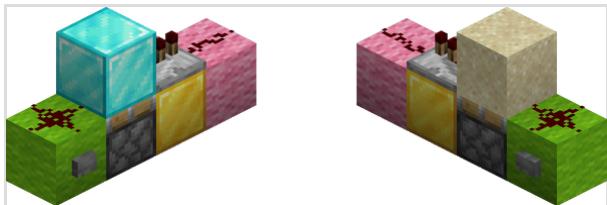Variations: The output repeater may be set to any delay, which also lengthens the output pulse to equal the delay. When oriented north-south, the output repeater may be replaced by any [mechanism component](#), causing the mechanism component to receive a 0 tick pulse.



Circuit Breaker Pulse Generator – Left: Sticky piston. Right: Regular piston. [schematic]


Observer Pulse generator

*1×1×3 (3 block volume), 1-wide, 1 high, tileable
circuit delay: 2 ticks
output pulse: 1 tick*

The observer pulse generator is one of the most common pulse generators due to its adaptability. It can be oriented in almost any direction, and the observer can be oriented in almost any direction, allowing for lots of flexibility. And depending on where the output is taken

from, it can be a rising or falling edge pulse generator. The observer can also be updated by other circuitry to send more pulses from the output.

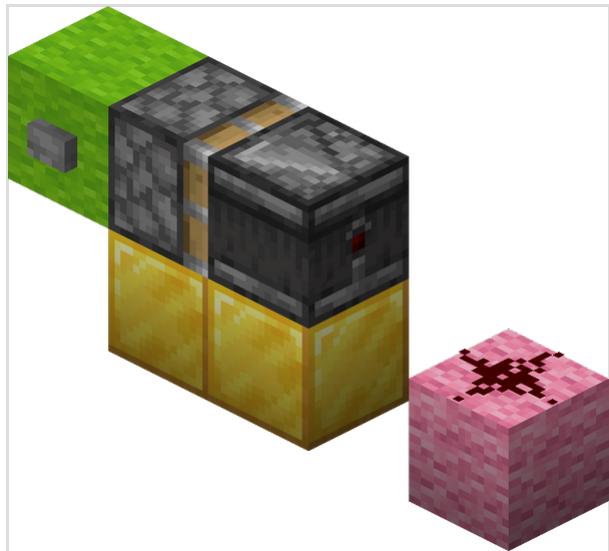Variations: The piston base can be oriented in any way; the same is true for the observer except for facing the piston itself. Output can be taken from either the extended or retracted position to change which edge it activates on.




common observer pulse generator

Dust-Cut Pulse Generator

*1×4×3 (12 block volume), 1-wide
circuit delay: 0 ticks
output pulse: 1.5 tick*

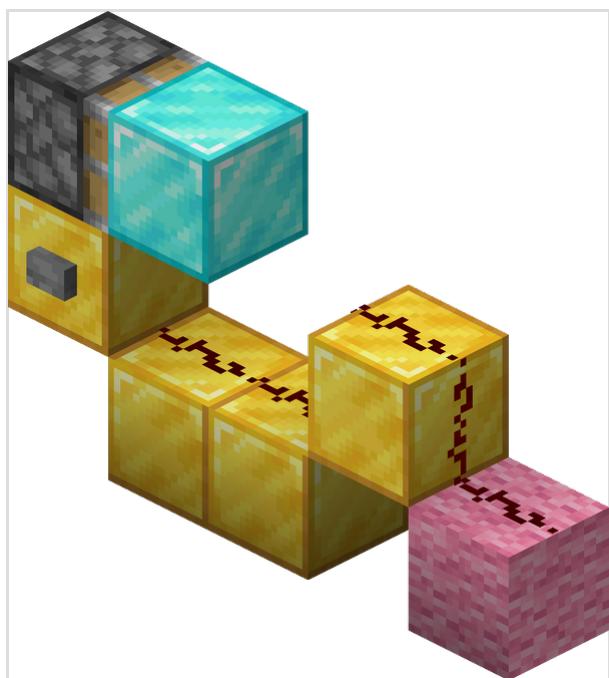A dust-cut pulse generator limits the output pulse by moving a block so that it cuts the output dust line.



Dust-Cut Pulse Generator – [schematic]


NOR-Gate Pulse Generator

*1×4×3 (12 block volume), 1-wide, silent
circuit delay: 2 ticks
output pulse: 1 tick*

A NOR-gate pulse generator compares the current power to the power from 2 ticks ago – if

the current power is on and the previous power was off, the output torch flashes on briefly.

This design uses a trick to limit the output pulse to a single tick. A redstone torch cannot be activated by a 1-tick pulse from exterior sources, but a torch activated by a 2-tick exterior pulse can short-circuit itself into a 1-tick pulse. To increase the output pulse to 2 ticks, remove the block over the output torch. To then increase it to 3 ticks, increase the delay on the repeater to 4 ticks.

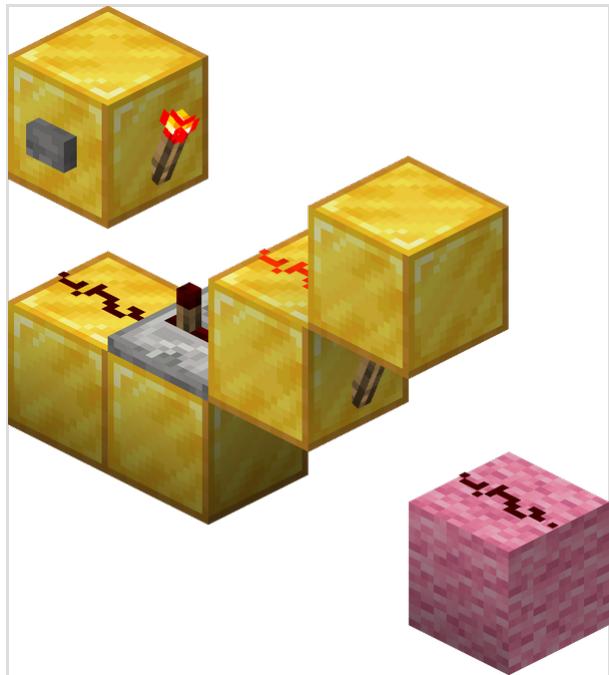


NOR-Gate Pulse Generator – [schematic]

Locked-Repeater Pulse Generator

*2×3×2 (12 block volume), flat, silent circuit delay: 2 ticks
output pulse: 1 tick*

When the lever is turned *off*, the locked repeater allows a pulse through.

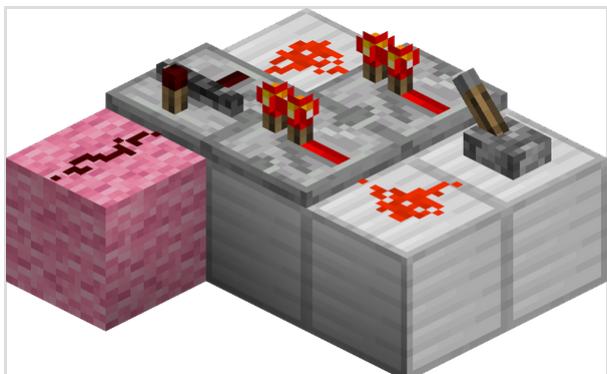Variations: The locked repeater and the input repeaters can be set to any delay. This increases the output pulse length, but also the circuit delay.



Locked-Repeater Pulse Generator – [schematic]

Comparator-Repeater Pulse Generator

*2×4×2 (15 block volume), flat, silent circuit delay: 1 tick
output pulse: 2 ticks*

The dust first powers the comparator, turning on the output, then the delayed pulse (with the repeater) shuts off the output.

Variations: The repeater can be set to any number of ticks, increasing only the output pulse length.


Off-pulse Generator

An **off-pulse generator** has an output which is usually on, but generates an off-pulse when triggered.


OR-Gate Off-Pulse Generator

*1×3×3 (9 block volume), 1-wide, silent
circuit delay: 1 tick
output pulse: 1 tick (off)*

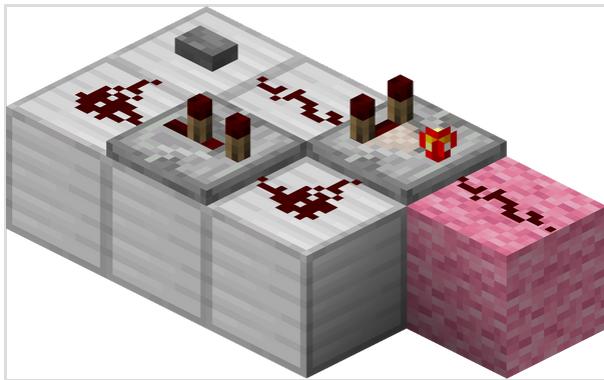When triggered, the bottom torch turns off, but the top torch doesn't turn on until 1 tick later, allowing a 1-tick off-pulse output.



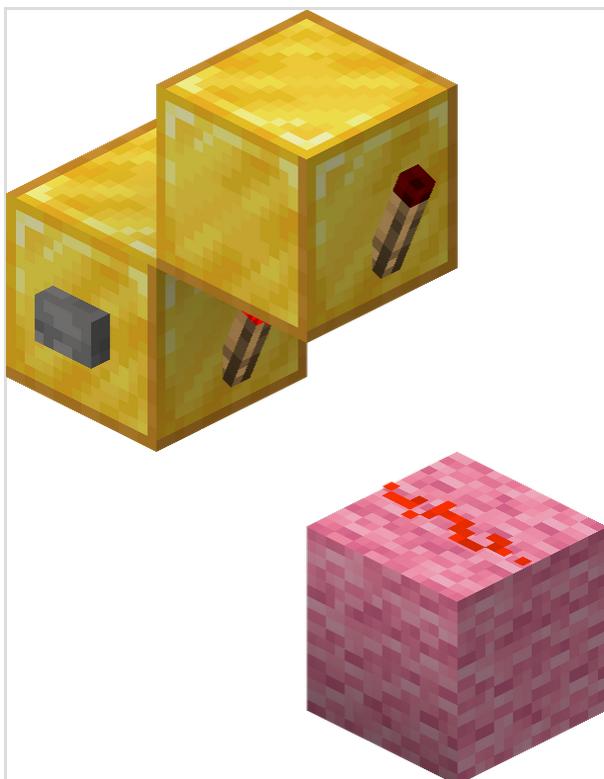Comparator-Repeater Pulse Generator - [schematic]



OR-Gate Off-Pulse Generator – [schematic]

Pulse length limiter

A **pulse limiter** (aka "pulse shortener") reduces the length of a long pulse.

An **ideal pulse limiter** would allow shorter pulses through unchanged, but in practice the range of input pulse can often be determined (or guessed) and it is sufficient to use a circuit which produces a specific pulse shorter than expected input pulses.

Any rising edge detector can also be used as a pulse limiter.


Schematic Gallery: Pulse Limiter

Circuit Breaker Pulse Limiter

*1×3×3 (9 block volume), 1-wide
circuit delay: 1 tick
output pulse: 1 tick*

The circuit breaker is the most commonly used pulse limiter due to its small size and adjustable output.

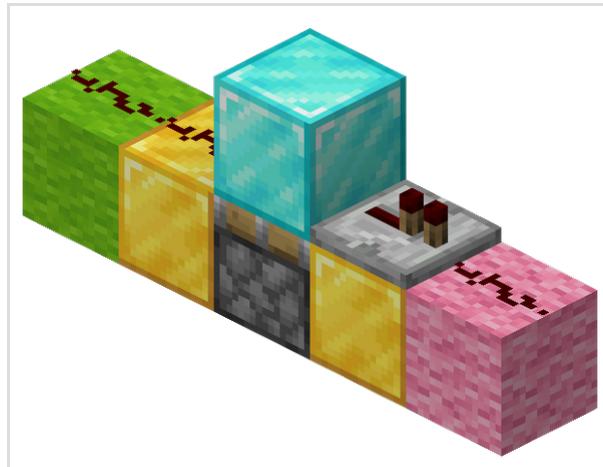Variations: The output repeater may be set to any delay, which also lengthens the output pulse to equal the delay. The output repeater may be replaced by any mechanism component, causing the mechanism component to receive a 0.5-tick activation pulse.



Circuit Breaker Pulse Limiter – [schematic]

Dust-cut pulse limiter

*1×5×3 (15 block volume), 1-wide,
instant
circuit delay: 0 ticks
output pulse: 1.5 tick*

A dust-cut pulse limiter limits the output pulse by moving a block so that it cuts the output dust line.

The dust-cut pulse limiter doesn't "repeat" its input (boost it back up to full power), so a repeater may be needed before or after it (adding delay).

The dust-cut pulse limiter is an "ideal" pulse limiter (see above). Pulses that are 1 tick or shorter (its maximum output pulse) are allowed through unchanged.




Dust-Cut Pulse Limiter – [schematic]

Moved-block pulse limiter

*3×3×2 (12 block volume), flat
circuit delay: 1 tick
output pulse: 0 ticks*

Uses the same principle as the circuit breaker pulse limiter – power the output through a block, then remove the block to keep the output pulse short.

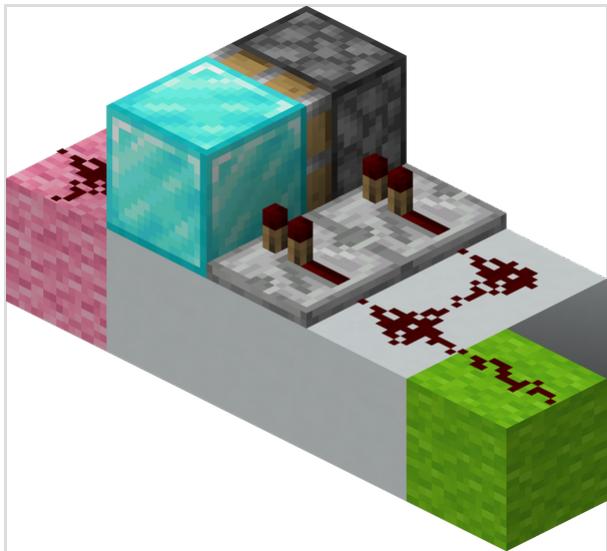Variations: The repeater powering the piston can be set to a longer delay to produce output pulses of 1, 2 or 3 ticks; it can also be replaced with a comparator to generate a 0-tick pulse that can reliably power other pistons



Moved-Block Pulse Limiter – [schematic]

NOR-gate pulse limiter

features vary (see [schematics](#))

A NOR-gate pulse limiter compares the current power to the power from 2 ticks ago – if the current power is on and the previous power was off, the output torch flashes on briefly.

Variations: Remove the block over the output torch to increase the pulse to 2 ticks.



NOR-Gate Pulse Limiter – (1-wide) [schematic]



NOR-Gate Pulse Limiter – Top: 1-tick. Bottom: Flat. [\[schematic\]](#)

Locked-repeater pulse limiter

*2×4×2 (16 block volume), flat, silent
circuit delay: 3 ticks
output pulse: 1 tick*

Uses repeater locking to shut pulses off after 1 tick.

Variations: The output repeater can set to any delay. This increases the output pulse, but also increases the circuit delay.

If the input doesn't have to be at the same height as the output, you can move the torch so that it's attached to the top of the block it's currently above, and run the input into that block (making the circuit only 2×3×2).



Locked-Repeater Pulse Limiter – [\[schematic\]](#)

Dropper-hopper pulse limiter

*1×4×2 (8 block volume), 1-wide, flat, silent
circuit delay: 3 ticks
output pulse: 3.5 ticks*

When the input turns on, the dropper pushes an item into the hopper, activating the comparator until the hopper pushes the item back.

The initial block is required to activate the dropper without powering it (which would deactivate the adjacent hopper, preventing it from returning the item to turn off the output pulse).

Because the output comes from a comparator used as an inventory counter, the output

power level is 1 (with a stackable item) or 3 (with a non-stackable item) – add a repeater for a higher power level output.

Variations: If the input and output don't need to be at the same height, you can reduce the size of the circuit by putting the hopper on top of the dropper (making the circuit 1×3×2).



Dropper-Hopper Pulse Limiter – [schematic]

Off-pulse limiter

An **off-pulse limiter** (aka "inverted pulse limiter") has an output which is usually on, but which shortens the length of long off-pulses.

Any inverted falling edge detector can also be used as an off-pulse limiter.

OR-gate off-pulse limiter


features vary (see schematics)

An or-gate off-pulse limiter combines the input with a delayed inverted input to limit off-pulses.


The "instant" version doesn't repeat its input (boost it back up to full power), so a repeater may be needed before or after it (adding delay).

Variations: The bottom repeater of the flat version can be adjusted to any delay, increasing the length of the off-pulse to match the repeater's delay (this doesn't actually increase the circuit delay).

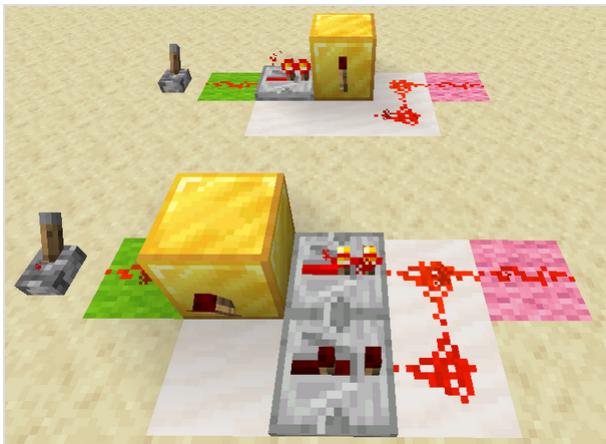The bottom redstone dust in the "instant" version can be replaced with a repeater to increase the length of its off-pulse.



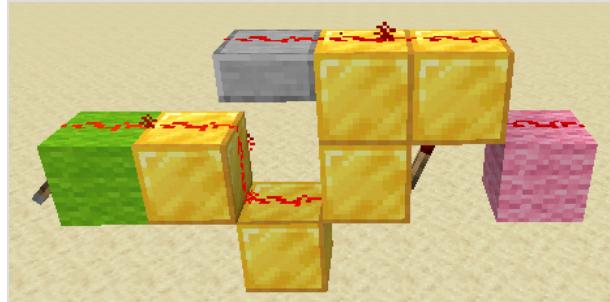OR-Gate Off-Pulse Limiter – Top: 1-tick. Bottom: Flat. [schematic]




OR-Gate Off-Pulse Limiter – Instant. [schematic]

Moving-block off-pulse limiter

*1×4×2 (8 block volume), 1-wide, instant
circuit delay: 0 ticks
output pulse: 2.5 ticks*

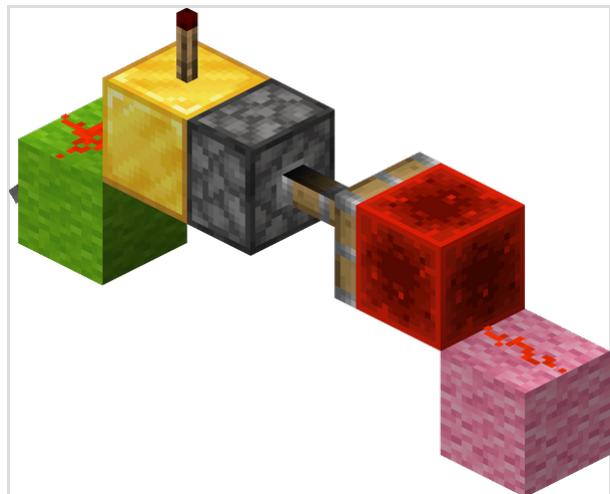When the input turns off, the piston begins to retract. 1 tick later, the torch turns on, which re-activates the sticky piston by quasi-connectivity, causing it to extend again.



Moving-Block Off-Pulse Limiter – [schematic]

Pulse extender

A **pulse extender** (a.k.a. "pulse sustainer", "pulse lengthener") increases the duration of a pulse.

The most compact options are:

- Up to 4 ticks: [Repeater](#)
- Up to 4 ticks per repeater: [Repeater-Line Pulse Extender](#)
- 1 second to 4 minutes: [Dropper-Latch Pulse Extender](#) or [Hopper-Clock Pulse Extender](#)
- 5 minutes to 81 hours: [MHDC Pulse Extender](#)

Schematic Gallery: Pulse Extender

Redstone repeater

1×1×2 (2 block volume)

1-wide, flat, silent

circuit delay: 1 to 4 ticks

output pulse: 1 to 4 ticks

For any input pulse shorter than its delay, a [redstone repeater](#) increases the duration of the pulse to match its delay. For example, a 3-tick repeater turns a 1-tick pulse or a 2-tick pulse into a 3-tick pulse.

Additional repeaters only delay the pulse, not extend it (but see the [repeater-line pulse extender](#) below).

Repeater-line pulse Extender


2×N×2

flat, silent, instant

circuit delay: 0 ticks (instant) or 4 ticks (delayed)

output pulse: up to 4 ticks per repeater

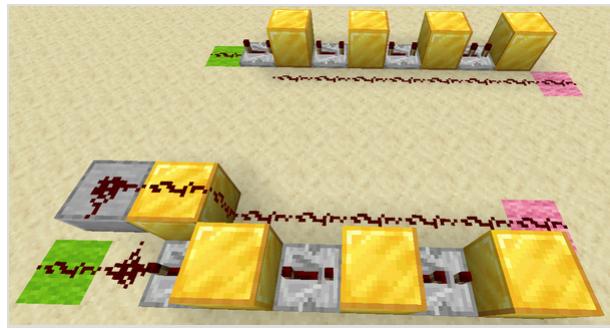For the instant version, the input must be a pulse at least as long as the longest-delay repeater in the line (usually 4 ticks) – if not, use the delayed version.



Repeater-Line Pulse Extender – Top: Delayed (1.4 second). **Bottom:** Instant (1 second).

[schematic]

Dropper-latch pulse extender

2×6×2 (24 block volume)

flat, silent

circuit delay: 5 ticks

output pulse: 5 ticks to 256 seconds

Each item in the middle hopper adds 8 ticks (0.8 seconds) to the output pulse. The output pulse can be fine-tuned by increasing delay on any repeater (or both) by up to 3 ticks or by replacing the repeater facing the hopper with a solid block to decrease the delay by 1 tick (these adjustments affect the *total* pulse duration, not per item, allowing pulse durations of any tick amount from 5 ticks to 256 seconds).



Dropper-latch pulse extender – [schematic]

Variations: If the input pulse might be longer than half the output pulse, add a block before the dropper to keep it from deactivating the hopper. A 1-wide version is possible by using two droppers (adjustable only in increments of 8 ticks):

1-wide dropper-latch pulse ?
extender
1×7×3 (21 block volume)
1-wide
<i>circuit delay:</i> 4 ticks
<i>output pulse:</i> 4 ticks to 256 seconds
The left dropper contains a single item and the left hopper contains one to 320 items.

Hopper-clock pulse extender

features vary (see [schematics](#))

circuit delay: 1 tick

output pulse: 4 ticks to 256 seconds


A **hopper-clock pulse extender** is a hopper clock with one of the sticky pistons replaced with a regular piston so that it doesn't pull the block of redstone back, but instead wait for the input to trigger a new clock cycle.

A hopper-clock pulse extender with a single item in its hoppers produces a 4-tick output pulse. Each additional item adds 8 ticks to the output pulse (unlike the [dropper-latch pulse extender](#), the output of a hopper-clock pulse extender can be adjusted only in 8-tick increments).

While waiting for the input to turn on, the sticky piston is actually in a state where it is powered but doesn't know it (like a stuck-piston BUD circuit) until "woken up" by the input changing its power level. This works as long as the input power level is different than the resting output of the powered comparator (unintuitively, it even works if the input power level is *less* than the comparator output).

Caveats:

- Any block or redstone update near the powered & stuck sticky piston can trigger it, so care should be taken to keep other circuit activity away from the sticky piston.
- The timer/counter part starts after the rising edge of the input pulse. -> At worst the output pulse is only "*input_pulse + extender_time/2*" not "*input_pulse + extender_time*". For "*input_pulse < extender_time/2*" it's always just "*extender_time*".

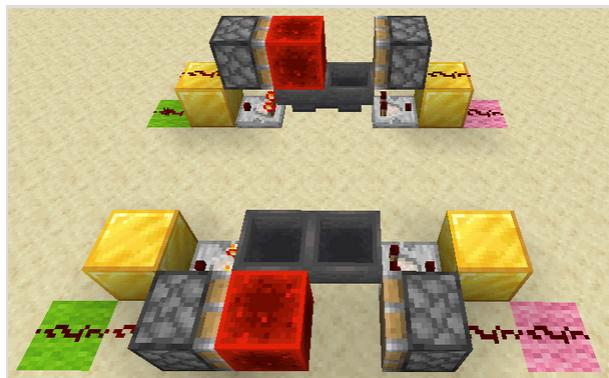

Hopper-Clock Pulse Extender – Top: 1-wide.
Bottom: Flat. In both, the left piston is sticky and the right is regular. [\[schematic\]](#)

Earliest known publication: 4 May 2013 CodeCrafted: "Minecraft QASi: Compact adjustable pulse extender" (<https://youtube.com/watch?v=v5PN35YRDDQ>) (based on the ethonian hopper clock)


RS latch pulse extender

features vary (see [schematics](#))

output pulse: up to 8 ticks per repeater

An **RS latch pulse extender** works by setting the output on with a latch, then resetting the latch after some delay.

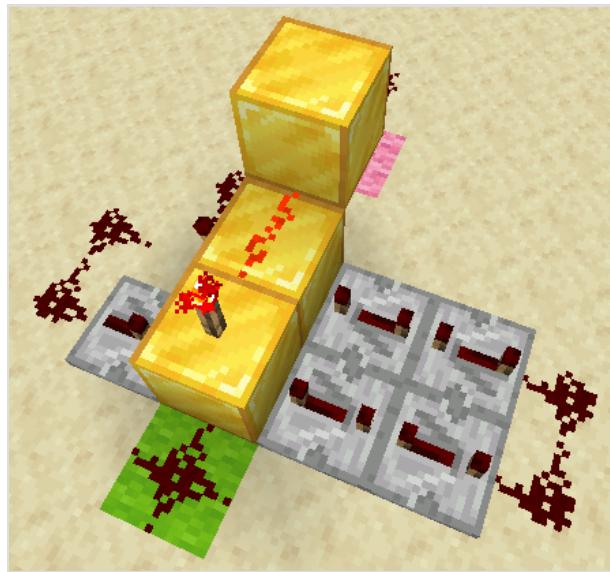Both of the circuits below use a trick to double the delay produced by the repeaters, by first powering the output from the latch, then from the repeaters. This means that any 1-tick adjustment to the repeater loop produces a 2-tick adjustment in the output pulse.



RS NOR Latch Pulse Extender (3 seconds) –

There is redstone dust under the raised block.

[[schematic](#)]

Fader pulse extender


$2 \times N \times 2$

flat, silent

circuit delay: 0 ticks

output pulse: input pulse + up to 15 ticks per comparator

The delay depends on the input's signal strength – for input signal strength S, the pulse is extended by S ticks per comparator. The signal strength of the output gradually decays, so should usually be boosted with a repeater. The design requires a certain minimum input pulse length, equal to 1 tick per comparator; shorter pulses will instead cause the device to repeat the pulse S times (for a total of S+1 pulses) at decaying signal strength.

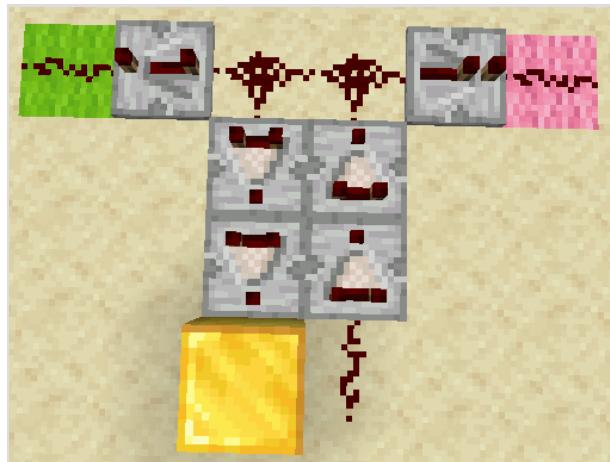

Fader Pulse Extender (6 seconds) – [[schematic](#)]

MHC pulse extender

$6 \times 6 \times 2$ (72 block volume)

flat

circuit delay: 3 ticks


output pulse: up to 22 hours

"MHC" stands for "multiplicative hopper clock" (a hopper counter multiplies the clock period of a hopper clock).

When the input turns on, the torch turns off, allowing both clocks to cycle into a state where the bottom clock continues to hold the torch off until it's completed one full cycle. The number of items in the top hoppers determines the top clock's cycle period, and its block of redstone moves every half-cycle, allowing the bottom clock to move one item.

The half-cycle is equal to the number of items in the top hoppers times 4 ticks (or 0.4 seconds per item) – up to 128 seconds for 320 items. The bottom clock keeps the output on for a number of half-cycles equal to twice the number of items in the bottom hoppers, minus 1. Thus, the output pulse equals $0.4 \text{ seconds} \times \langle \text{top items} \rangle \times (2 \times \langle \text{bottom items} \rangle - 1)$.

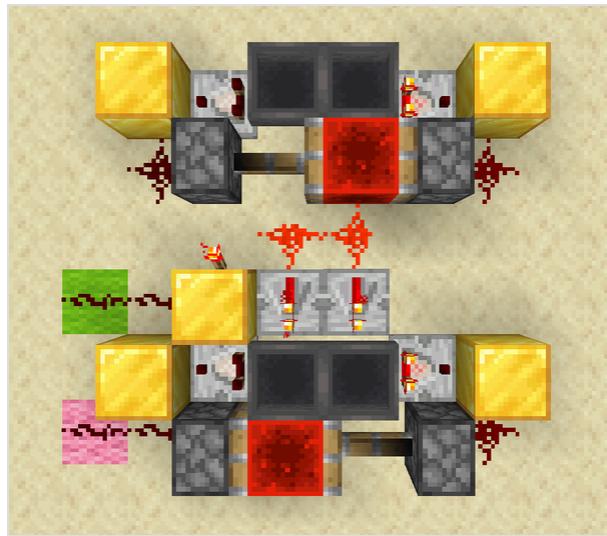Items Required for Useful Output Pulses [\[show\]](#)



MHC Pulse Extender – All pistons are sticky.
[[schematic](#)]

MHDC pulse extender

5×7×2 (70 block volume)

flat


circuit delay: 5 ticks

output pulse: up to 81 hours

"MHDC" stands for "multiplicative hopper-dropper clock" (a dropper counter multiplies the clock period of a hopper clock).

When the input turns on, the torch turns off, allowing both clocks to cycle into a state where the bottom clock continues to hold the torch off until it's completed one full cycle. The hoppers can hold up to 320 items (X) and the droppers can hold up to 576 items (Y). The duration of the output pulse is $X \times (2Y-1) \times 0.8 \text{ seconds}$.

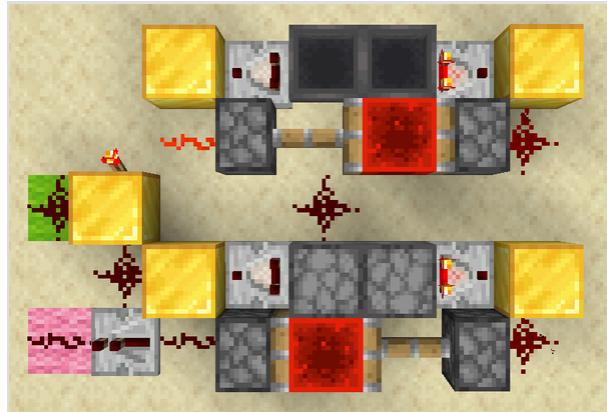Items Required for Useful Output Pulses [\[show\]](#)



MHDC Pulse Extender – All pistons are sticky.
[[schematic](#)]

Cooldown pulse extender

! Note: This circuit uses command blocks which cannot be obtained legitimately in survival mode. This circuit is intended for server ops and adventure map builds.

1×4×2 (8 block volume)


circuit delay: 3 ticks

output pulse: up to 27 minutes

This pulse extender uses a command block to slow the hopper transfer rate. The exact command depends on the direction the pulse extender is facing, but for a pulse extender facing the positive X direction it looks something like this: /data modify block ~2 ~ ~

TransferCooldown set value X, where X is the number of game ticks (up to 32,767) to hold the item in the hopper (20 game ticks = 1 second, lag permitting).

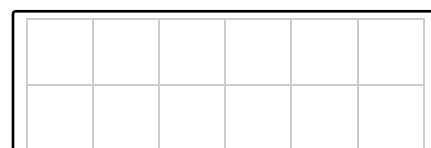When the command block is powered directly it activates the adjacent dropper, pushing the item into the hopper to power the output, and simultaneously changes the hopper's cooldown time to delay when it pushes the item back to the dropper.



Cooldown pulse extender

— The dropper contains a single item.

Pulse multiplier

A **pulse multiplier** turns one input pulse into multiple output pulses.

There are three primary strategies for designing pulse multipliers:

- Split the input pulse into multiple paths that arrive at the output at different times
- Enable a clock to run while the input pulse is on
- Trigger a clock that runs for a finite number of cycles, independent of the input pulse length


In case the player requires only the pulse frequency to be doubled, usually a simple dual edge detector is often sufficient:

Observer pulse doubler

1×1×1 (1 block), flat, silent, 1-tileable

circuit delay: 1 tick

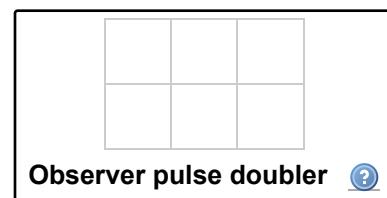output pulses: 2 1-tick pulses the length of input pulse apart.



Observer pulse doubler

An observer watching the input signal (redstone dust, button, repeater set to 1 tick, etc) produces a pulse on each of the edges of the input, producing two 1-tick pulses on each edge of the input pulse, providing the input pulse is sufficiently long (3 redstone ticks minimum). If the pulse is shorter than this, a redstone lamp can be put in front of the observer to remedy this issue.

Schematic Gallery: Pulse Multiplier

Split-path pulse multiplier

A **split-path pulse multiplier** produces multiple pulses by splitting the input signal into multiple paths and having them arrive at the output at different times. This usually requires first reducing the length of the input pulse with a pulse length limiter to reduce the delay required between each output pulse.

Dispenser double-pulser

*1×6×3 (18 blocks), 1-wide
circuit delay: 1 tick
output pulses: 1 tick and 2 ticks*

This circuit is useful for double-pulsing a dispenser, to quickly dispense then retract water or lava. First it powers a block on one side of the dispenser, then the other side.



Dispenser Double-Pulser – [schematic]

Enabled-clock pulse multiplier

An **enabled-clock pulse multiplier** runs a clock for as long as the input stays on, thus producing a number of pulses relative to the input pulse length.

Subtraction 1-clock pulse multiplier

*2×3×2 (12 blocks), flat, silent
circuit delay: 1 tick
output pulses: 1 tick*

This pulse multiplier does not repeat its input signal, so may need a repeater before or after (increasing the circuit delay).

This circuit produces 5 pulses when enabled with a stone button, or 7 pulses when enabled with a wooden button. For other number of pulses, consider a pulse extender to lengthen the input pulse.



Subtraction 1-Clock Pulse Multiplier – [schematic]

Subtraction N-clock pulse multiplier

*2×3×2 (12 blocks), flat, silent
circuit delay: 1 tick
output pulses: 2+ ticks*

The output pulses are 1 tick longer than the delay set on the repeater (so, 2 to 5-tick output pulses). For even longer pulses, replace the dust next to the repeater with another repeater.

This pulse multiplier does not repeat its input signal, so may need a repeater before or after (increasing the circuit delay).

The table below shows the number of output pulses produced with various combinations of button inputs and repeater delays (for more pulses, consider a [pulse extender](#) to lengthen the input pulse):

Repeater Delay	Stone Button	Wooden Button
1 tick	3 pulses	4 pulses
2 ticks	2 pulses	3 pulses
3 ticks	2 pulses	2 pulses
4 ticks	1 pulse	2 pulses




Subtraction N-Clock Pulse Multiplier – [schematic]

Torch-repeater N-clock pulse multiplier

*2×4×2 (16 blocks), flat, silent
circuit delay: 2 ticks
output pulses: 3+ ticks*

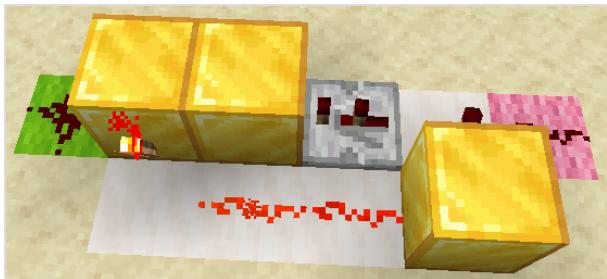The output pulses are 1 tick longer than the delay set on the repeater (so, 3 to 5-tick output pulses). The repeater can't be set to a 1-tick delay or the right torch burns out (which could be useful for limiting the number of pulses to 8 maximum).



Torch-Repeater N-Clock Pulse Multiplier – [schematic]

Triggered-clock pulse multiplier

A **triggered-clock pulse multiplier** consists of a clock circuit that is allowed to run for a specific number of cycles once triggered. Strategies for designing a triggered-clock pulse multiplier include using a latch to turn the clock on and have the clock itself reset the latch back off after one or one-half clock cycles, or using a pulse extender to run a clock.

Dropper-latch 2-clock pulse multiplier

*3×4×2 (24 blocks), flat, silent
circuit delay: 3 ticks
output pulses: 1 to 320 2-tick pulses*

This pulse multiplier produce one 2-tick pulse for every item placed in the bottom dropper

(with a 2-tick off-pulse between each on-pulse).

After it has finished its pulses, it requires a reset time equal to $0.4 \text{ seconds} \times \text{pulse count}$. If it is reactivated during this time, it produces fewer pulses.

If the input pulse is longer than the output pulses, the powered dropper prevents the clock from turning off because the disabled hopper can't push its item back. If a long input pulse is possible, place a solid block between the input and the dropper so that it activates without being powered.

Earliest known publication: 4 September 2013 [1]

As of 1.11, the lower hopper needs a longer pulse from the clock.

To compensate, we add a repeater facing down to a block next to the, now below the dropper, hopper, and set it to 3 ticks.

If you want a longer clock, use the formula: $2n - 1$ where n is the clock pulse, for the delay of the lower repeater



Dropper-Latch 2-Clock Pulse Multiplier – The top dropper contains a single item. The bottom dropper contains a number of items equal to the desired pulse count. [\[schematic\]](#)



Dropper-Latch 2-Clock Pulse Multiplier (Updated) Added a repeater for the lower hopper to compensate and lock the items while active


Dropper-latch 1-clock pulse multiplier

$2 \times 9 \times 2$ (36 blocks), flat, silent
circuit delay: 5 ticks
output pulses: 2 to 777 1-tick pulses

This pulse multiplier allows a wide range of pulses, with no reset time required.

The first and last items placed in the middle hopper should be non-stackable items (to give the output enough signal strength to run the subtraction clock). Up to three stacks of stackable items may be placed between the two non-stackable items.

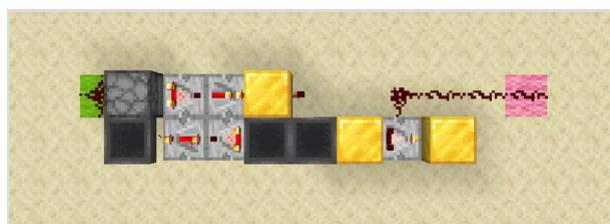The circuit produces four 1-tick pulses for every item placed in the middle hopper (with a 1-tick off-pulse between each on-pulse). The total number of pulses may be reduced by 1 by changing the 4-tick repeater to 2 ticks, or reduced by 2 by replacing the 4-tick repeater with



Dropper-Latch 1-Clock Pulse Multiplier – The dropper contains a single item. The middle hopper contains one or more items depending on the desired pulse count (the first and last items should be non-stackable items). [\[schematic\]](#)

a block, or increased by 1 by changing the 1-tick repeater to 3 ticks.

If the input pulse is longer than the output pulses, the powered dropper prevents the clock from turning off because the disabled hopper can't push its item back. If a long input pulse is possible, place a solid block between the input and the dropper so that it activates without being powered.

Pulse divider

A **pulse divider** (a.k.a. "pulse counter") produces an output pulse after a specific number of input pulses – in other words, it turns multiple input pulses into one output pulse.

Because a pulse divider must count the input pulses to know when to produce an output pulse, it has some similarity to a ring counter (an n -state memory circuit with only one state on). The difference is that a ring counter's output state changes only when its internal count is changed by an input trigger, while a pulse divider produces an output pulse and then returns to the same unpowered output it had before its count was reached (in other words, a pulse divider is monostable but a ring counter is bistable). Any ring counter can be converted into a pulse divider just by adding a pulse limiter to its output (making it monostable).

In addition to the circuits here, a clock multiplier can function as a pulse divider (or a ring counter, for that matter); unlike these circuits, its output remains ON until the next input pulse turns it off.

Schematic Gallery: Pulse Divider

Hopper-loop pulse divider

$2 \times (3 + \text{pulse count}/2) \times 3$
output pulse: 3 ticks

This is a hopper-loop ring counter with an incorporated pulse limiter on the output.

Each input pulse turns the redstone dust off for 1 tick, allowing the item to move to the next hopper. When the item reaches the dropper it turns on the output briefly, until the redstone dust turning back on activates the dropper to push the item to the next hopper.

To count an even number of pulses, replace another hopper with a dropper. Putting the second dropper right before the first dropper changes the output pulse to 6 ticks.

The output is signal strength 1 or 3 (with a stackable or non-stackable item in the hoppers) so may need to be boosted with a repeater.

Variations: Removing the dust from on top of the dropper and replacing the dropper with a



Hopper-Loop Pulse Divider – [schematic]

hopper increases the output pulse to 4 ticks but makes the entire circuit silent.

Dropper-hopper pulse divider

$3 \times 4 \times 2$ (24 block volume)
flat
output pulse: $(4 \times \text{pulse count})$ ticks

The dropper-hopper pulse divider can count up to 320 pulses.

Each input pulse pushes an item from the dropper to the hopper next to it. When the dropper is finally emptied, its comparator turns off, allowing the item in the bottom-left hopper to move to the right, starting the reset process. When the top hopper has finished moving items back to the dropper, the item in the bottom hoppers moves back to the left, ending the reset process.

Once it has begun its output pulse, the pulse divider goes through a reset period of $(4 \times \text{pulse count})$ ticks (the same length as the output pulse). Any new input pulses during the reset period is not counted, but only extends the reset period. Because of this reset period, this pulse divider is best when the typical interval between input pulses is greater than the reset period, or you can run a line back from the output to suppress inputs while it is resetting.

The output is signal strength 1 or 3 (with a stackable or non-stackable item in the bottom hoppers) so may need to be boosted with a repeater. The output pulse length is also proportional to the pulse count, so may need to be shortened with a [pulse limiter](#).




Dropper-Hopper Pulse Divider – The dropper contains a number of items equal to the pulse count. The bottom-left hopper contains a single item. [\[schematic\]](#)

Dropper-dropper pulse divider

$3 \times 6 \times 2$ (36 block volume)
flat
output pulse: $(2 \times \text{pulse count})$ ticks

The dropper-dropper pulse divider can count up to 576 pulses.

Each input pulse pushes an item from the left dropper to the right dropper. When the left dropper is finally emptied, its comparator turns off, allowing the item in the bottom-left hopper to move to the right, starting the subtraction 1-clock driving the reset process (although the subtraction clock pulses the dropper, the circuit's output alternates only in signal strength, staying on the whole time – subtraction clocks can be tricky that way!). When the right dropper has

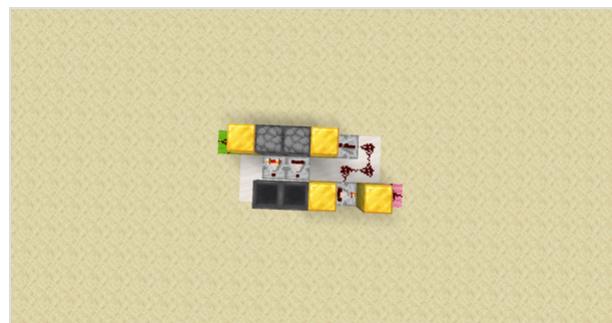

Dropper-Dropper Pulse Divider – The left dropper contains a number of items equal to the pulse count. The left hopper contains a single non-stackable item. [\[schematic\]](#)

finished moving items back to the left dropper, the item in the bottom hoppers moves back to the left, ending the reset process.

Once it has begun its output pulse, the pulse divider goes through a reset period of $(2 \times \text{pulse count})$ ticks (the same length as the output pulse). Any new input pulses during the reset period is not counted, but only extends the reset period. Because of this reset period, this pulse divider is best when the typical interval between input pulses is greater than the reset period, or you can run a line back from the output to suppress inputs while it is resetting.

The output alternates between signal strength 1 and 3 so may need to be boosted with a repeater. The output pulse length is also proportional to the pulse count, so may need to be shortened with a pulse limiter.

Inverted binary divider or counter


3×5×2 (30 block volume)
flat, silent, 3-wide stackable
(alternating)
 input: 2 off-ticks, use a pulse limiter if necessary
output pulse: 2 off-ticks
delay: 3 ticks (per unit in stack)

The inverted binary divider or counter uses the latching feature of redstone repeaters to create a two-state (binary) counter. Multiple counters can be stacked to construct an n -bit counter, giving 2^n input pulses per output pulse. It is called 'inverted' because it counts the number of *off* pulses, rather than on-pulses. Note that it triggers every two off-ticks, so holding the input low causes it to count multiple times then burn out a redstone torch. You may want to use a pulse limiter on the input signal to prevent this.


Used purely as a pulse divider or counter this circuit is somewhat inefficient, since it would have to be stacked nine times to be able to count almost as many pulses (512) as the dropper-dropper divider. However, the stacking binary design means that the pulse count value can be easily read out by simply taking an output line from each stack element. In combination with OR or NOR gates, this can be used to trigger an output after an arbitrary number of pulses, or to create a divider for any number when combined with the reset circuit below.

'Tall' binary counter

2×5×3 (30 block volume)

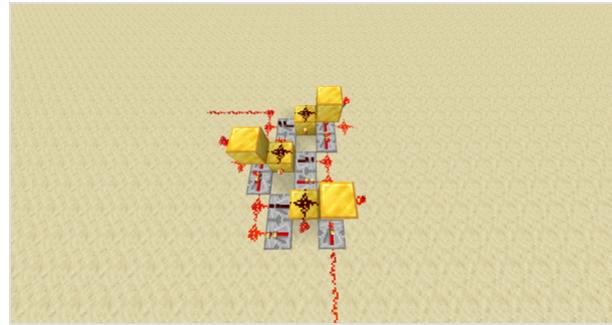

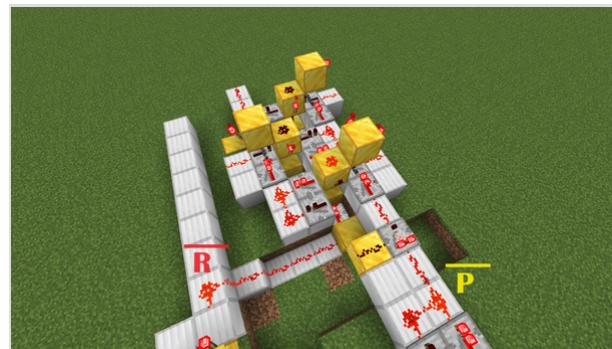Binary Counter (Tall) – Three dividers stacked to make an 8-counter. [schematic]



Binary Counter with Reset [schematic]

silent, 2-wide stackable (alternating)

Functionally the same as the flat ($3 \times 5 \times 2$) binary counter, but takes one extra vertical block and one less horizontally, which may be an advantage when stacking them together. Requires an extra torch compared to the flat circuit.

Binary counter reset circuit


Adding this to the binary counter circuit allows it to be reset at any time; this can be used to create a counter for any desired number, or even a programmable counter (with extra circuits to select the number). This can be applied to either version, though the schematic shows it connected to the 'tall' version.

Like the counter itself, the reset circuit is *active low*; it requires at least three off-ticks to perform the reset, although the actual reset does not take place until the rising edge (end) of the off-pulse. (A standard button followed by an inverter works fine, as seen in the screenshot.)

1-tick binary counter/divider [Java Edition only]

$1 \times 3 \times 2n+1$ (1-tick input) or $1 \times 3 \times 2n+3$ (for input longer than 1 tick)
1-wide, tileable
 2^n divider
output pulse: 1-4 ticks

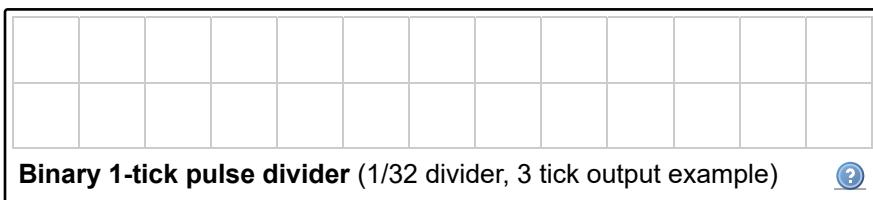A cheap, noisy option to output 1 out of 2^n pulses (1 in 2, 4, 8, 16, 32 etc.), indefinitely extensible - each next module (repeater-piston pair) doubling the divider.



Depends on the Java Edition's quirk of sticky pistons 'spitting out' their payload when activated with 1-tick pulses and quasi-connectivity. If the input pulse is longer than 1 tick, the first module acts as pulse limiter instead of a 'memory cell', so the only modification needed for this sort of input is adding one more module vs 1-ticked input (e.g. from an observer). The output pulse can be extended up to 4 ticks by increasing the tick count on the last repeater.

Use as a binary counter requires reading position of the blocks moved by the pistons, e.g. through repeaters one block above the 'rest' position.

If the input has mixed length pulses, both 1-tick and longer, set the first repeater to 2 ticks and treat the first piston as pulse limiter, not counter module.

Edge detector

An **edge detector** outputs a pulse when it detects a specific change in its input.

- A rising edge detector outputs a pulse when the input turns on.
- A falling edge detector outputs a pulse when the input turns off.

- A dual edge detector outputs a pulse when the input changes.

An **inverted edge detector** is usually on, but outputs an off-pulse (it turns off, then back on again) when it detects a specific change in its input.

- An inverted rising edge detector outputs an off-pulse when the input turns on.
- An inverted falling edge detector outputs an off-pulse when the input turns off.
- An inverted dual edge detector outputs an off-pulse when the input changes.

Circuit	Rising Edge	Falling Edge
Rising Edge Detector	On-pulse	n/a
Falling Edge Detector	n/a	On-pulse
Dual Edge Detector	On-pulse	On-pulse
Inverted Rising Edge Detector	off-pulse	n/a
Inverted Falling Edge Detector	n/a	off-pulse
Inverted Dual Edge Detector	off-pulse	off-pulse

Rising edge detector

A **rising edge detector** (RED) outputs a pulse when its input turns on (the *rising edge* of the input).

Any rising edge detector can also be used as a pulse generator or pulse limiter.


Schematic Gallery: Rising Edge Detector

Circuit breaker

1×3×3 (9 block volume)
1-wide
circuit delay: 1 tick
output pulse: 1 tick

The circuit breaker is one of the most commonly used rising edge detector due to its small size and adjustable output.

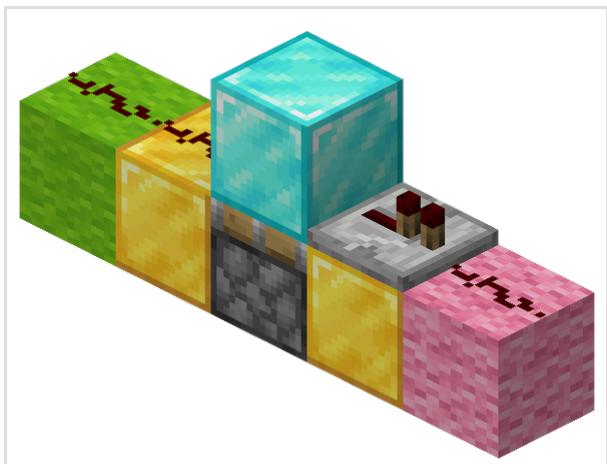Variations: The output repeater may be set to any delay, which also lengthens the output pulse to equal the delay. When oriented north-south, the output repeater may be replaced by any mechanism component, causing the mechanism component to receive a 0-tick activation pulse.



Circuit Breaker – [schematic]

Moved observer RED


1x1x3, 1x1x1, 1x2x2
1-wide, 1-wide flat, flat
circuit delay: Java: 2 ticks, Bedrock: 4 ticks

output pulse: 1 tick

This observer pulse edge detector is one of the most common edge detectors due to its modifiability. It can be oriented in almost any direction, and the observer can be oriented in almost any direction, allowing for lots of flexibility. And depending on where the output is taken from, it can be a rising or falling edge pulse generator. The observer can also be updated by other circuitry to send more pulses from the output.

Variations: The piston base can be oriented in any way, the observer can be oriented in any way except for facing the piston. Output can be taken from either the extended or retracted position to change which edge it activates on.

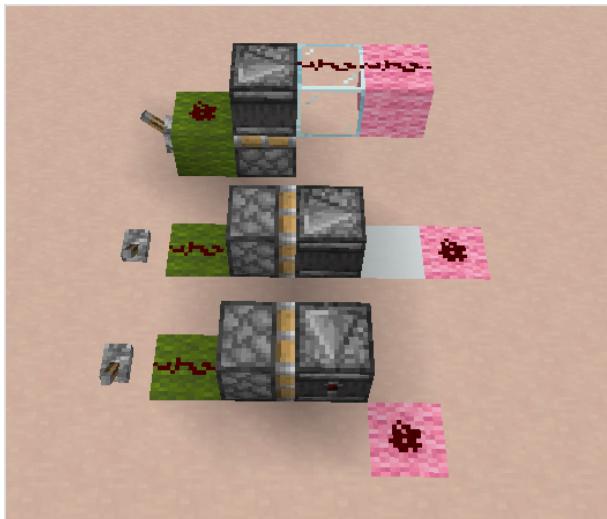Works both with standard binary and pulse logic. [Java Edition only]



Moved Observer RED variants (vertical, straight, angled)

Dust-cut rising edge detector

1×5×3 (15 block volume)

1-wide, instant

circuit delay: 0 ticks ("Unrepeated") or 1 tick ("Repeated")

output pulse: 1 tick, 1.5 ticks if the output is a piston

A dust-cut rising edge detector works by moving a block so that it cuts the output dust line after only one tick.

Because of the output's fractional length, a 1-tick repeater may be needed to force a sticky piston to drop its block.



Dust-Cut RED (Unrepeated) – [schematic]



Dust-Cut RED (Repeated) – [schematic]

Subtraction rising edge detector

2×4×2 (16 block volume)

flat, silent

circuit delay: 1 tick ("Unrepeated") or 2 ticks ("Repeated")

output pulse: 1 tick

A subtraction rising edge detector works by using the subtraction mode of a redstone comparator to shut off the output pulse.


This design uses a trick to limit the output pulse to a single tick. A comparator can't produce a 1-tick pulse by subtraction from an exterior source (such as if the repeater was set to a 1-tick delay), but if the external source would usually produce a 2-tick pulse or more, the comparator can short-circuit itself into a 1-tick pulse by incorporating it into a subtraction 1-clock (the block and parallel dust after the comparator), but allowing the clock to run for only one cycle.

Variations: Remove the final block and dust to increase the output pulse to 2 ticks. Then increase the delay on the subtraction repeater to increase the output pulse length further.

Earliest known publication: 7 January 2013 (basic concept)^[2] and 3 May 2013 (1-tick output refinement)^[3]



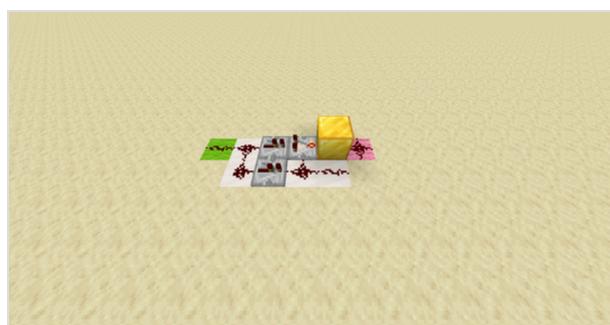Subtraction RED (Unrepeated) – [schematic]



Subtraction RED (Repeated) – [schematic]

Locked-repeater rising edge detector

2×4×2 (16 block volume)

flat, silent

circuit delay: 3 ticks


output pulse: 1 tick

Uses repeater locking to shut pulses off after 1 tick.

Variations: If the input doesn't have to be at the same height as the output, you can move the torch so that it's attached to the top of the block it's currently above, and run the input into that block.



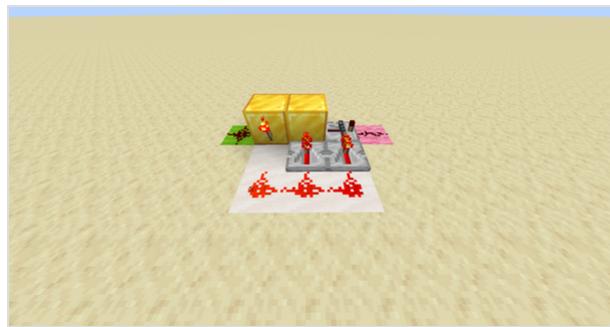Locked-Repeater RED (Corner) – [schematic]



Locked-Repeater RED (In-line) – [schematic]

Dropper-hopper rising edge detector

1×4×2 (8 block volume)
1-wide, silent
circuit delay: 3 ticks
output pulse: 3.5 ticks

When the input turns on, the dropper pushes an item into the hopper, activating the comparator until the hopper pushes the item back.

The initial block is required to activate the dropper without powering it (which would deactivate the adjacent hopper, preventing it from returning the item to turn off the output pulse).

Because the output comes from a comparator used as an inventory counter, the output power level is 1 (with a stackable item) or 3 (with a non-stackable item) – add a repeater for a higher power level output.

Variations: You can reduce the size of the circuit by putting the hopper on top of the dropper.



Dropper-Hopper RED – [schematic]


Moved-block rising edge detector

3×3×2 (18 block volume)
flat
circuit delay: 1 tick
output pulse: 1 tick


Uses the same principle as the circuit breaker – power the output through a block, then remove the block to keep the output pulse short.

Variations: To increase the output pulse length, increase the delay on the repeater powering the piston. To get a 0-tick pulse, replace the repeater powering the piston with a comparator

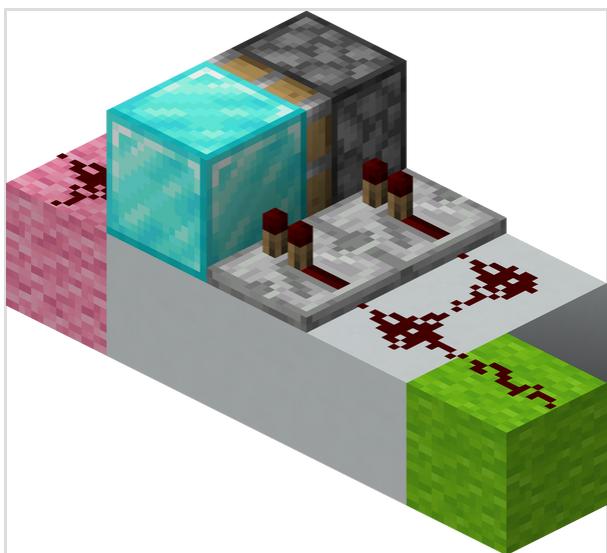
Other variations start with the piston powered. The output of the "offset" variation is weakly-powered and requires a repeater or comparator to do anything other than activate a mechanism component.



Moved-Block RED – [schematic]

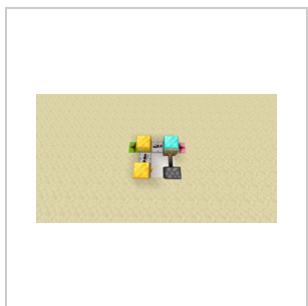

Moved-Block RED
(In-line)

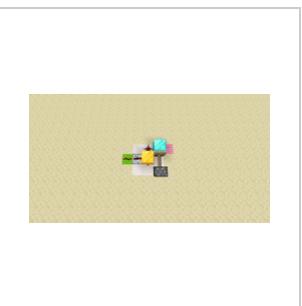

Moved-Block RED
(Offset)

Earliest known publication: 14 March 2013^[4] and 29 March 2013^[5]


NOR-gate rising edge detector

1×4×3 (12 block volume)
1-wide, silent
circuit delay: 2 ticks
output pulse: 1 tick

A NOR-gate rising edge detector compares the current power to the power from 2 ticks ago – if the current power is on and the previous power was off, the output torch flashes on briefly.

All of these designs use a trick to limit the output pulse to a single tick. A redstone torch cannot be activated by a 1-tick pulse from exterior sources, but a torch activated by a 2-

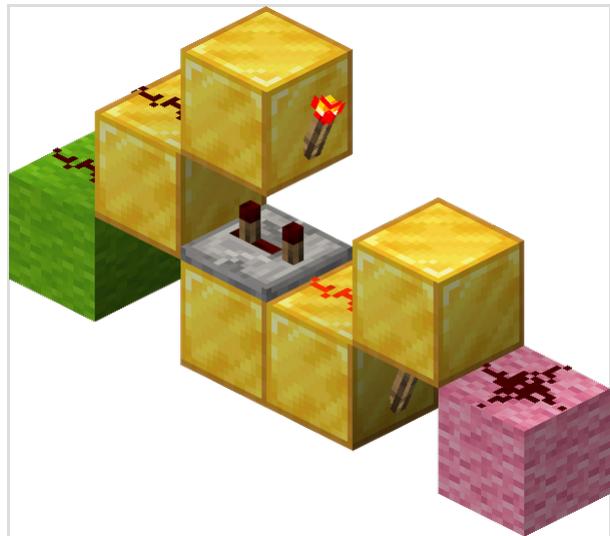tick exterior pulse can short-circuit itself into a 1-tick pulse. Remove the block over an output torch to increase the output pulse to 2 ticks.



NOR-Gate RED – [\[schematic\]](#)

Falling edge detector

A **falling edge detector** (FED) outputs a pulse when its input turns off (the *falling edge* of the input).

Schematic Gallery: Falling Edge Detector

Dust-cut falling edge detector

1×4×3 (12 block volume)
1-wide, instant
circuit delay: 0 ticks
output pulse: 2 ticks

When the input turns off, the piston immediately retracts the block, allowing the still-powered repeater to output a signal for 2 ticks. When the input turns on again, the piston cuts the connection before the signal can get through the repeater.



Dust-Cut FED – [\[schematic\]](#)

Moved-block falling edge Detector

1×3×3 (9 block volume)
1-wide
circuit delay: 1 ticks
output pulse: 1 ticks

For some directions and input methods, the repeater may be needed to be set to 3 ticks to

operate mechanism components.

Earliest known publication: 27 May 2013^[6]



Moved-Block FED – [schematic]

Moved-observer FED

1×2×3 (6 block volume)

1-wide

circuit delay: Java: 2 ticks, Bedrock: 4 ticks


output pulse: 1 tick

This circuit uses a sticky piston and an observer to separate the rising from the falling edge of a signal. The rising edge powers the piston, lifting the observer above the redstone where it has no effect. Then, at the falling edge of the input signal, the piston retracts and the observer sends a 1-tick pulse via the redstone on the glass block. Note that the glass block is required to prevent this from turning into a clock.

Variations: The piston base can be oriented in any way, the observer can be oriented in any way except for facing the piston. Output can be taken from either the extended or retracted position to change which edge it activates on.



Moved Observer FED - 1-wide

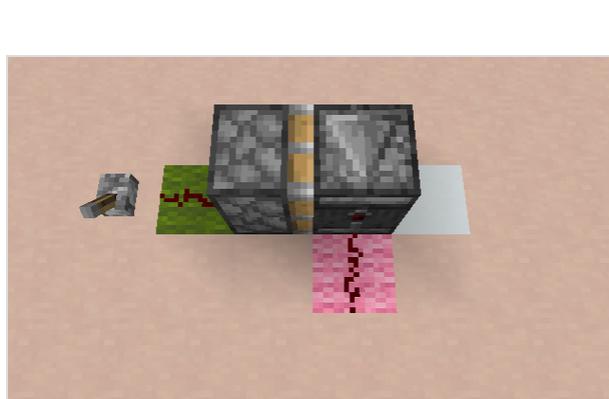

Moved Observer FED - flat

Locked-hopper falling edge detector

1×4×2 (8 block volume)

1-wide, silent

circuit delay: 1 tick

output pulse: 4 ticks

When the input turns off, it takes 1 tick for the torch to turn back on, giving hopper A a

chance to push its item to the right and activate the output.

This circuit requires time to reset (to push the item back into hopper A), so the fastest input clock it can handle is a 4-clock.

Because the output comes from a comparator used as an inventory counter, the output power level is 1 (with a stackable item) or 3 (with a non-stackable item). Add a repeater for a higher power level output.

Variations: This circuit can be snaked around in many different ways as long as the input dust is able to deactivate the first hopper.

Earliest known publication: 22 May 2013^[7]




Locked-Hopper FED – [schematic]

Locked-repeater falling edge detector

2×3×2 (12 block volume)
flat, silent
circuit delay: 2 ticks
output pulse: 1 tick

When the input turns on, the output repeater is locked before it can be powered by the block behind it. When the input turns off, the output repeater is unlocked and is briefly powered by the block behind it, producing a 1-tick output pulse.

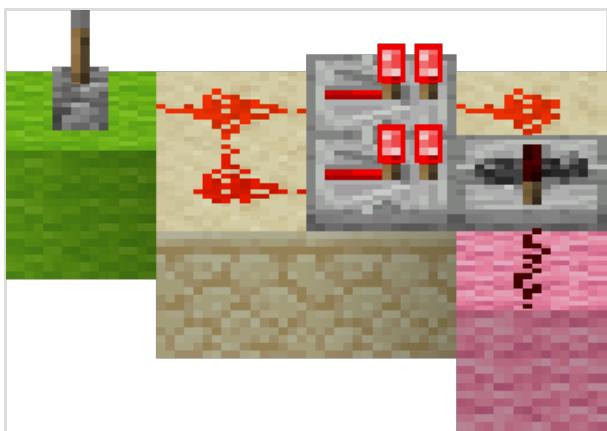Variations: Increase the delay on the output repeater to increase the output pulse length (up to 4 ticks), but also the circuit delay.




Locked-Repeater FED – [schematic]

Subtraction falling edge detector

2×5×2 (20 block volume)
flat, silent
circuit delay: 1 tick
output pulse: 1 tick

This design uses a trick to limit the output pulse to a single tick. A comparator can't produce a 1-tick pulse by subtraction from an exterior source (such as if the repeater was set to a 1-tick delay), but if the external source would usually produce a 2-tick pulse or more, the comparator can short-circuit itself into a 1-tick pulse by incorporating it into a subtraction 1-clock (the block and parallel dust after the comparator), but allowing the clock to run for only one cycle.

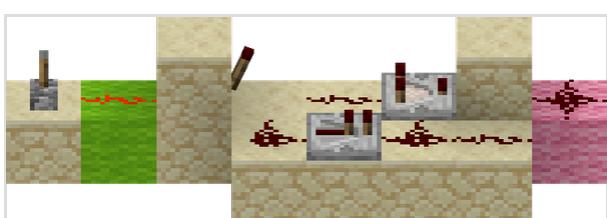

Subtraction FED – [schematic]

Variations: Remove the final block and the dust next to it for a 2-tick pulse, then increase the delay on the repeater for a 3 or 4-tick pulse.

NOR-gate falling edge detector

2×4×3 (24 block volume)

silent

circuit delay: 1 tick


output pulse: 1 tick

This circuit compares the current power to the power from 2 ticks ago – if the current power is off and the previous power was on, the output torch flashes on briefly.

This design uses a trick to limit the output pulse to a single tick. A redstone torch

cannot be activated by a 1-tick pulse from exterior sources, but a torch activated by a 2-tick exterior pulse can short-circuit itself into a 1-tick pulse.

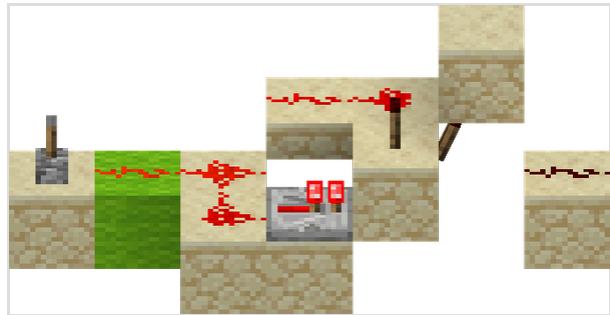Variations: Remove the block over the output torch to increase the output pulse to 2 ticks, then increase the delay on the repeater to increase the output pulse further.



NOR-Gate FED – [schematic]

Observer FED / RED


2x4x2, 1×4×3 or 1x5x3 (16, 12 or 15 block volume)

1-wide or flat, silent (tileable)

circuit delay: 2 tick

output pulse: 1 tick

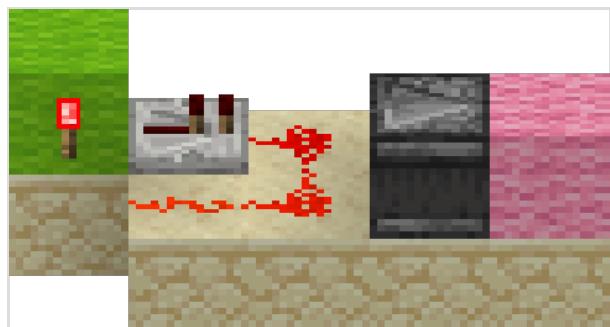The observer in this circuit only triggers when the input turns off due to repeaters having a higher tile tick priority than redstone torches. The "trick" is to keep the same distance between the observer to the repeaters output **and** the torch.




Observer FED - flat – [schematic]

Variations:

- Both flat and 1-wide versions allow for four different observer orientations.
 - Increase the repeater delay of the non-tileable variants to turn this FED into a RED.
 - The blue block in the tileable version is an inverted input to turn it into a RED.
- (by Nilbadimo)



Observer FED - 1-wide

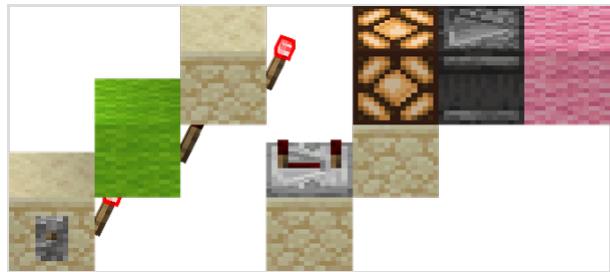

Observer FED - tileable

Dual edge detector

A **dual edge detector** (DED) outputs a pulse when its input changes (at either the rising edge or the falling edge of the input). The simplest way to do is using an observer.

Schematic Gallery: Dual Edge Detector

Moving-block dual edge detector

The block of redstone moves when the signal turns on and when it turns off. While it is moving it cannot power the redstone dust, so the output torch turns on until the block of redstone stops moving.

In the 1-wide version the block over the output torch short-circuits it into a 1-tick pulse – remove the block and take the output directly from the torch to increase the output pulse to 1.5 ticks. To get an output on the same side as the input, the torch can be placed on the other side of the bottom blocks (but without the block above it, which would clock the piston). The piston and block of redstone can be moved to the side of the dust, rather than on top of the dust, producing a shorter but wider circuit.

Earliest known publication: 28 January 2013^[8]

Dust-cut dual edge detector

features vary (see schematics)

The simple version splits the difference between a rising edge detector and a falling edge detector to produce an output of 1 tick on each edge. The instant version adds an unrepeatable rising edge detector to reduce the rising edge circuit delay to 0 ticks.

Locked-repeater dual edge detector

features vary (see schematics)

A locked-repeater dual edge detector uses the timing of repeater locking to detect signal edges.

The nor-gate design uses a trick to limit the output pulse to a single tick. A redstone torch cannot be activated by a 1-tick pulse from exterior sources, but a torch activated by a 2-

tick exterior pulse can short-circuit itself into a 1-tick pulse. Remove the block over the output torch (and the dust on the block it's attached to) to increase the output pulse to 3 ticks.

Earliest known publication: 16 April 2013 (NOR-gate locked-repeater FED)^[9] and 1 May 2013 (OR-gate locked-repeater FED)^[10]

Piston OR-gate dual edge detector

3×4×2 (24 block volume)

flat

circuit delay: 1.5 ticks

output pulse: 1.5 ticks

A piston OR-gate dual edge detector moves a block between repeaters that change states shortly after the piston moves. This causes a pulse to be sent to a wire behind the moving block.

Subtraction dual edge detector

features vary (see schematics)

A subtraction dual edge detector powers a comparator with an ABBA circuit, cutting the pulse short with subtraction.

Earliest known publication: 3 August 2013^[11]

Twin NOR-gate dual edge detector

The most trivial way to build a dual edge detector is to OR the outputs of a NOR-gate rising edge detector and a NOR-gate falling edge detector. A useful feature of this approach is that you get the rising- and falling-only pulses for free if you need them. If resource or space usage is more important than timing, parts of the components of the 2 single edge detectors can be shared (the middle row of the example in the Schematic Gallery: Dual Edge Detector). Again, the blocks above the torches limit the output pulse to 1 tick.

Inverted rising edge detector

An **inverted rising edge detector** (IRED) is a circuit whose output is usually *on*, but which outputs an off-pulse on the input's rising edge.

Schematic Gallery: Inverted Rising Edge Detector

OR-gate inverted rising edge detector

1×3×3 (9 block volume)

1-wide, silent

circuit delay: 1 tick

output pulse: 1 to 3 ticks (off-pulse)

An OR-gate inverted rising edge detector compares the current and previous input – if the current input is on and the previous input was off, the output turns off for a brief period.

Variations: The "adjustable" version takes up the same space, but its output pulse can be adjusted from 1 to 3 ticks. The "flat" version can also be adjusted from 1 to 3 ticks.



OR-Gate IRED – [schematic]



OR-Gate IRED
(Adjustable)



OR-Gate IRED (Flat)

Earliest known publication: 1 June 2013^[12]

Moving-block inverted rising edge detector

1×4×3 (12 block volume)

1-wide, instant

circuit delay: 0.5 ticks

output pulse: 1 tick (off-pulse)

This is a moving-block inverted dual edge detector with a repeater added to suppress the output on the falling edge.



Moving-Block IRED – [schematic]

Dropper-hopper inverted rising edge detector

1×3×3 (9 block volume)

1-wide, silent

circuit delay: 3 ticks


output pulse: 4 ticks (off-pulse)

When the input turns on, the dropper pushes the item up into the hopper, deactivating the comparator until the hopper pushes the item back down.

The initial block is required to activate the dropper without powering it (which would deactivate the adjacent hopper, preventing it from returning the item to turn the output pulse back on).

Because the output comes from a comparator used to measure inventory, the output power level is 1 (with a stackable item) or 2 (with a non-stackable item) – add a repeater for a higher power level output.

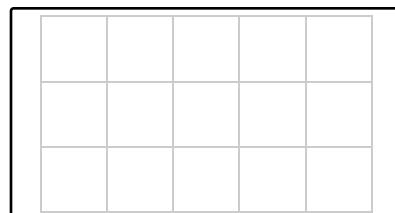Variations: The input block can be moved to the side of or underneath the dropper, and the hopper can be moved to the side of the dropper.



Dropper-hopper IFED – [?](#)

The dropper contains a single item.

Inverted falling edge detector

An **inverted falling edge detector** (IFED) is a circuit whose output is usually *on*, but which outputs an off-pulse on the input's falling edge.

Schematic Gallery: Inverted Falling Edge Detector

OR-gate inverted falling edge detector


features vary (see schematics below)

The input has two paths to the output, timed so that the output blinks off briefly when the input turns off.

Moved-block inverted falling edge detector

*1×4×2 (8 block volume), 1-wide, instant
circuit delay: 0 ticks, output pulse: 2.5 ticks (off-pulse)*

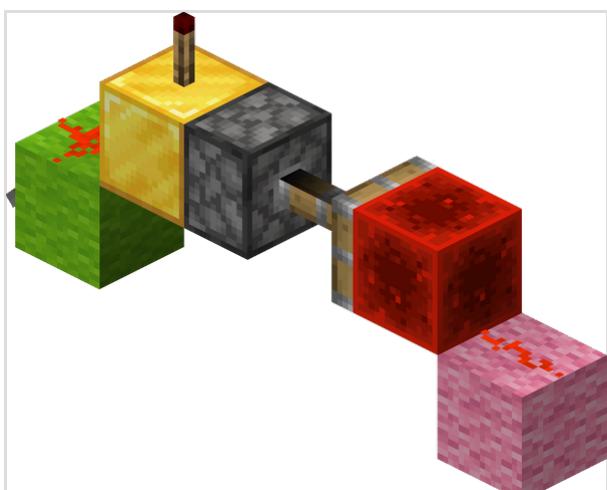Earliest known publication: 4 June 2013 [\[13\]](#)



Moved-Block IFED – [\[schematic\]](#)

Locked-repeater inverted falling edge detector

*2×3×2 (12 block volume), flat, silent
circuit delay: 2 ticks, output pulse: 1 tick (off-pulse)*

When the input turns on, the output repeater is locked before it can turn off. When the input turns off, the output repeater is unlocked and is briefly un-powered by the block behind it, producing a 1-tick output off-pulse.

Inverted dual edge detector

An **inverted dual edge detector** (IDED) is a circuit whose output is usually *on*, but which outputs an off-pulse when its input changes.

Schematic Gallery: Inverted Dual Edge Detector

Moving-block inverted dual edge detector

*1×3×3 (9 block volume), 1-wide, instant
circuit delay: 0 ticks, output pulse: 1.5 ticks (off-pulse)*

Variations: The piston and block of redstone can be moved to the side of the dust, rather than on top of the dust, producing a flat 2-wide circuit.

The sticky piston can be oriented vertically if the redstone dust is run around the side in a 2×2×4 configuration.

OR-gate inverted dual edge detector

*3×4×2 (24 block volume), flat, silent
circuit delay: 2 ticks, output pulse: 3 ticks (off-pulse)*

Uses the timing of repeater locking to detect pulse edges.

Slime BUD inverted dual edge detector

*1×3×4 (12 block volume)
circuit delay: instant, output pulse: 1 tick (off-pulse)*

The Slime BUD made possible by Minecraft 1.8 works great as an instant inverted dual-edge detector. Simply put a block of obsidian, a hopper, a furnace, etc. right next to the slime block, and run redstone from its top to your output, and put a piece of redstone dust on the same plane as the piston, with one block space between. That's your input.

Variations: move the obsidian (or whatever you used) -- and the redstone on top of it -- up one block to get a normal (non-inverted) dual edge detector, but with 1.5 ticks delay.

Pulse length detector


Sometimes it is useful to be able to detect the length of a pulse generated by another circuit, and

specifically whether it is longer or shorter than a given value. This has many uses, such as special combination locks (where the player have to hold down the button), or detecting [Morse code](#).

Long pulse detector

2×6×3 (36 block volume)
silent

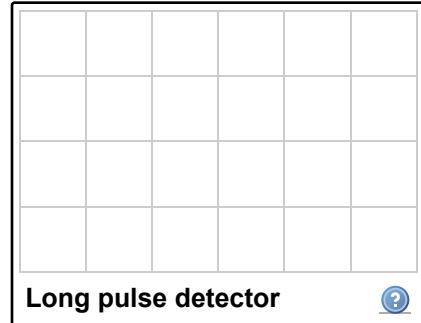
To test for a long pulse, we use an [AND gate](#) between the beginning and end of a line of [redstone repeaters](#). These allow the signal to pass through only if it has a signal length longer than the delay of the repeaters. A pulse that does get through is *shortened* by the delay amount, possibly down to 1 tick.



Long pulse detector


2×5×2 (20 block volume)
flat

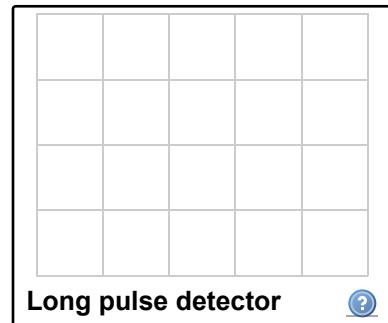Similar to the design above, but using a piston-based AND gate which shuts off the output as soon as the input turns off.



Pulse length differentiator

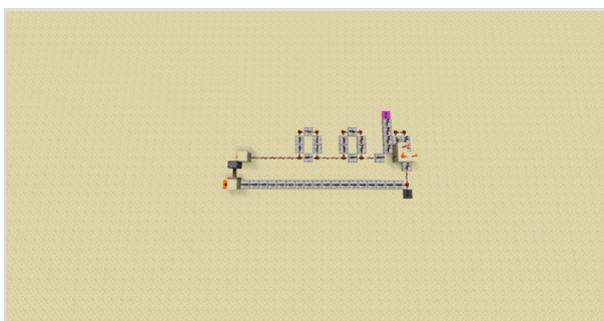A pulse length differentiator has two outputs and one input. Long pulses go through one output, while short pulses go to the other. It also keeps the tick length of the signals, which is why all the repeaters are set to one tick (i.e., a 1-tick signal remains a 1-tick signal). This is useful in a telegraph machine, in order to split up dashes and dots.




Input at gray wool, short output at orange wool,
long output at purple wool.

Transports and Logic gates implemented in Pulse logic

Some basic circuits exploiting the pulse logic. See the reference link for more advanced use of pulse logic circuitry.^[14]

Rail update transport

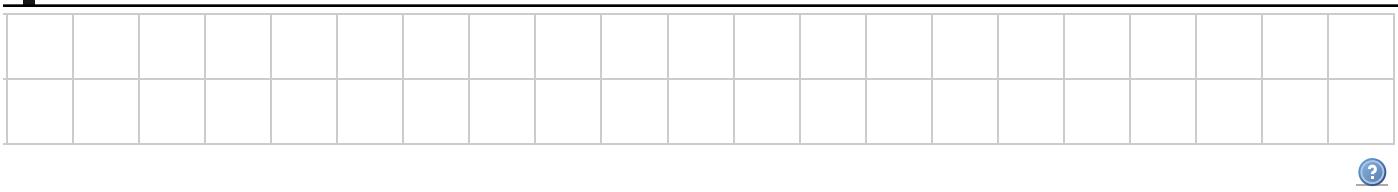[?](#)


1-tileable

Typically, in pulse logic circuitry, signal is sent over [Powered Rail](#) or [Activator Rail](#). Since the two don't propagate the updates to each other, this allows for tight tiling of modules.

NOT gate

1-tileable

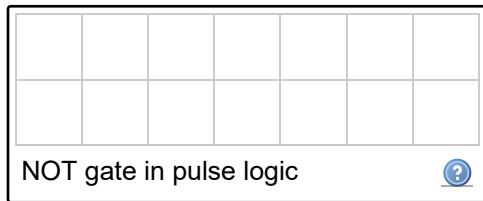Negation of signal depends only on initial position of blocks, or often - only on interpretation of the signals by the creator.




NOT gate in pulse logic

[?](#)

AND gate

1-tileable

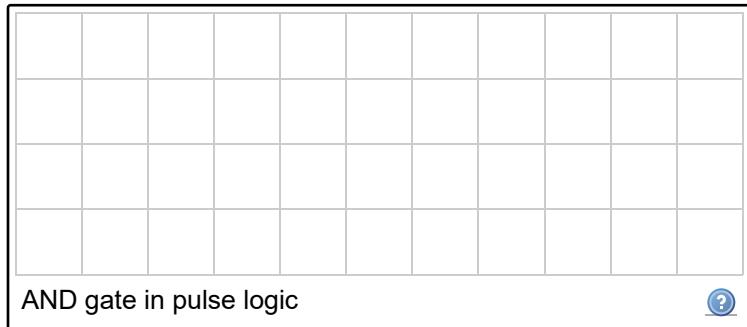


AND gate in pulse logic

[?](#)

OR gate

1-tileable

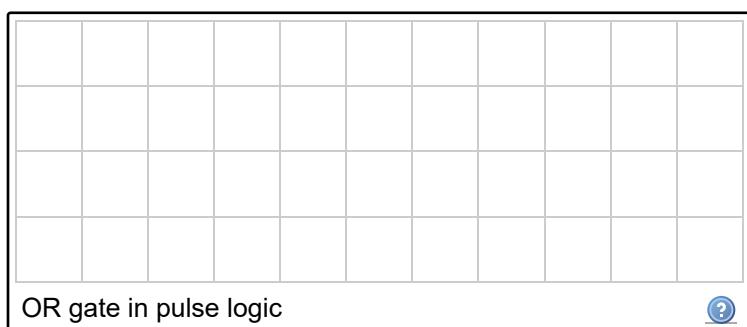The OR gate in pulse logic differs from AND gate only by initial positions of the blocks.




OR gate in pulse logic

[?](#)

XOR gate

1-tileable

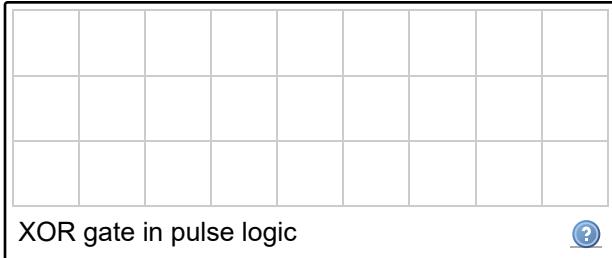
Generic redstone OR in pulse logic acts as XOR.



XOR gate in pulse logic




Leaf block update transport

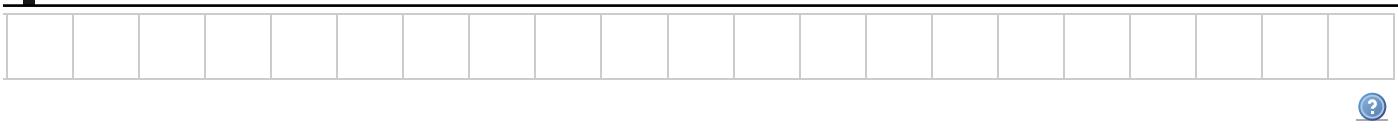

1-wide

The "greenstone" or "leafstone" transport depends on updates of leaf blocks depending on changing distance from the nearest log block. This transport is particularly helpful in transporting signal upward and downward. Updates do propagate to neighboring blocks though, and take 1 game tick to progress to next block. It makes it useful in creating 1 gametick resolution timing source though.

Scaffolding block update transport

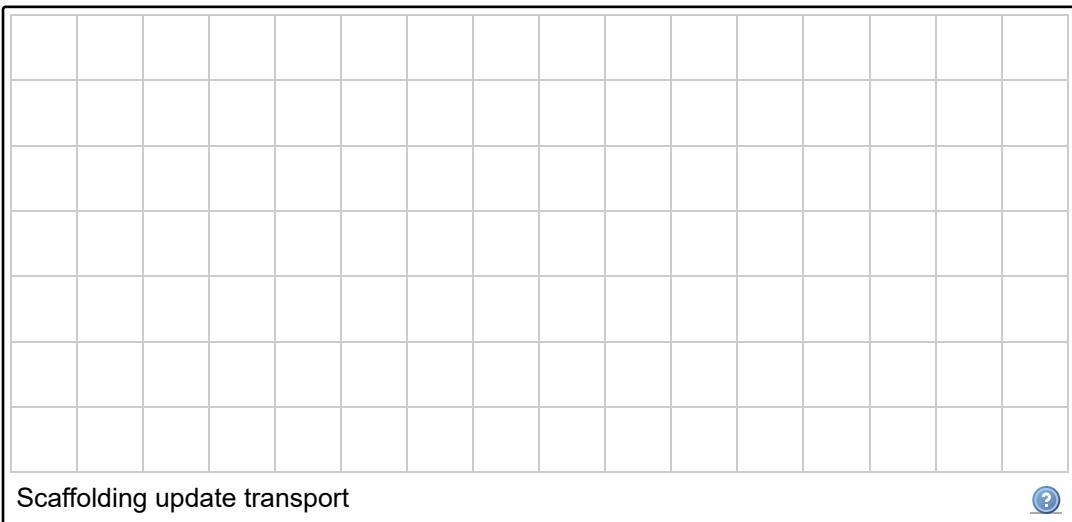

Scaffolding update transport




The Scaffolding propagates updates containing distance from supported scaffolding block. By moving a block under a suspended section of scaffolding, the player can send a signal an arbitrary distance upward and up to six blocks horizontally in any direction. The signal propagates at 1 block per redstone tick.

Wall block update transport

1 tick regardless of distance, 1-tileable (see caveat)

Wall blocks (cobblestone wall etc.) instantly transmit signal arbitrary distance down by turning themselves and all wall block below from smooth wall segment to a pillar segment if certain blocks are placed on them or attached from a side. To form a smooth segment, a wall needs two other wall blocks or other blocks wall can attach to, adjacent to it from two opposite sides. If they are other wall blocks though, it doesn't matter if they are smooth or pillars - so the solution is 1-tileable, but requires uninterrupted columns of full blocks (or wall) on far ends. Probably the most practical way to toggle a wall between these states is a redstone-controlled trapdoor. The readout through an observer is possible only from below though, as the wall connects to an observer from a side.

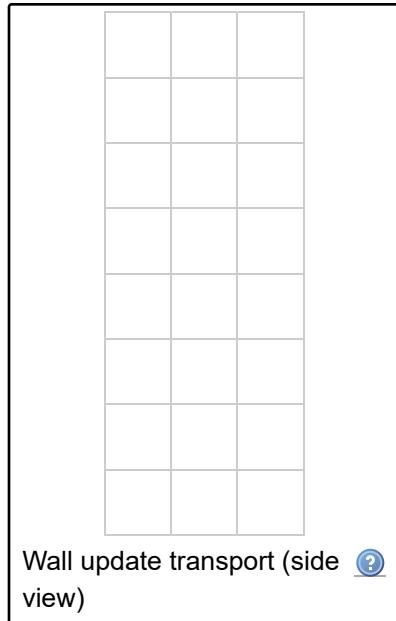

References




1. "RedsMiners" (4 September 2013). "Pulse multiplier 2.0" (<https://www.youtube.com/watch?v=HXK7C9cscd4>) (Video). *YouTube*.
2. "CarlitoxGamex" (7 January 2013). "Limitador de pulso Snapshot 1.5.2 / 1.5.1 con Redstone Comparator" (<https://www.youtube.com/watch?v=a8-dGX21CeY>) (Video). *YouTube*.
3. "NiceMarkMC" (3 May 2013). "Minecraft - Silent 1 Tick Pulse Generator" (<https://www.youtube.com/watch?v=31vHV-yJsRE>) (Video). *YouTube*.
4. "Goklayeh" (14 March 2013). "looking for Ver 1.5 pulse limiter designs" (<https://www.minecraftforum.net/topic/1726597-looking-for-ver-15-pulse-limiter-designs/#entry21407225>) (Post #3). *Minecraft Forum*.
5. "RamblinWreckGT" (29 March 2013). "Monostable Circuits and Sticky Pistons in 1.5.1" (<https://www.minecraftforum.net/topic/1747353-monostable-circuits-and-sticky-pistons-in-151/#entry21673572>) (Post #3). *Minecraft Forum*.
6. "fennoman12" (27 May 2013). "Extremely small falling edge monostable | Redstone with Feno" (<https://www.youtube.com/watch?v=028iQMMRboU>) (Video). *YouTube*.
7. "shufflepower" (22 May 2013). "compact falling edge detector i created/ "A compact falling edge detector I created..." (<http://www.reddit.com/r/redstone/comments/1euys6/a>). *Reddit*.
8. "Redstone Sheep" (28 January 2013). "Super simple dual edge monostable" (<https://www.youtube.com/watch?v=8HoJVf3iy78>) (Video). *YouTube*.
9. ""Selulance" (16 April 2013). "Dual Edge Detector using locking repeaters" (<https://www.minecraftforum.net/topic/1773409-dual-edge-detector-using-locking-repeaters/>) (Post #5). *Minecraft Forum*.
10. "sfpeterm" (1 May 2013). flat dual edge detector extremely simple/ "Silent & Flat Dual Edge Detector [extremely simple]" (<http://www.reddit.com/r/redstone/comments/1dgisq/silent>). *Reddit*.
11. ""leetmoaf" (3 August 2013). believe what i made is a pulse limiter but im/ "I believe what I made is a pulse limiter. But I'm not 100% sure." (<https://www.reddit.com/r/MinecraftInventions/comments/1jmakw/i>). *Reddit*.





12. "Cozzmy13" (1 June 2013). 3x1x2 pulse shortener/ "Small 3x1x2 pulse shortener" (<https://www.reddit.com/r/redstone/comments/1fgaje/small>). *Reddit*.
13. "ImETtheAlien" (4 June 2013). "How to make simple compact fast redstone pulsers in Minecraft 1.5.2! [Tutorial] Works in 1.6!" (<https://www.youtube.com/watch?v=R1SzyjE6BW4>) (Video). *YouTube*.
14. Pallapalla (2 December, 2017). "Observer logic: 1 Wide tillable logic gates + most compact adder?" (<https://www.youtube.com/watch?v=l8zXAJX-swA&list=PLynaxRWBkT09aSV3DDckLPDCV1aBY7xO7>) (Video). *YouTube*.

Navigation

 **Redstone** [hide]
Redstone circuits & tutorials [hide]

Redstone basics  Redstone components  Redstone mechanics  Conductivity

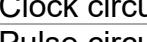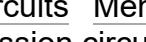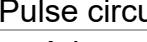Redstone circuits  Clock circuits  Logic circuits  Memory circuits  Miscellaneous circuits
 Pulse circuits  Transmission circuits

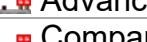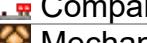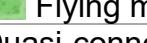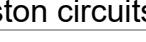Featured tutorials  Advanced redstone circuits  Block update detector (BUD)
 Comparator update detector (CUD)  Flying machine
 Mechanisms  Piston circuits  Quasi-connectivity
 Redstone music

Redstone components [show]

Retrieved from "https://minecraft.wiki/w/Redstone_circuits/Pulse?oldid=3318944"

This page was last edited on 14 December 2025, at 13:53.

Content on this site is licensed under CC BY-NC-SA 3.0 unless otherwise noted;
additional terms may apply.

Not an official Minecraft website. We are not associated with Mojang or Microsoft.